

2012.

一. (1) $U(t) = L(t) \frac{d i(t)}{dt} + i(t) \frac{d L(t)}{dt}$

(2) $L(t) > 0$ 且 $\dot{L}(t) \geq 0$.

证明: 同前


二. 解: (1)

$B_f = [-Q_t^T \quad 1_L]$

$Q_f = [1_L \quad -B_t^T]$

$B_f = [-Q_t^T \quad 1_L] = \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 & 9 & 10 & 11 \\ 1 & 1 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & -1 & 1 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 1 & -1 & 1 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 1 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & -1 & 0 & -1 & 0 & 0 & 0 & 0 & 1 & 0 \\ -1 & 0 & -1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix}$

(2)

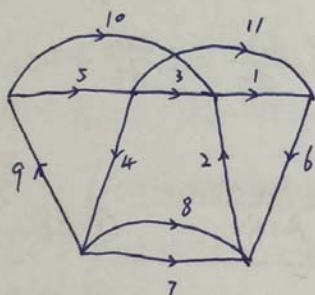

写回路, 按着堆积即可

同向为正, 反向为负.

三. 解: (1) CCCS 对原始不定导纳矩阵贡献:

$i_{43} = \beta i_{14} = \beta G_1 (u_1 - u_4)$ 即为: $4 \begin{bmatrix} \beta G_1 & -\beta G_1 \\ -\beta G_1 & \beta G_1 \end{bmatrix} = \begin{bmatrix} 1 & 4 \\ 3 & -2 \end{bmatrix}$

理想受压器

对原始不定导纳矩阵贡献:

$\begin{bmatrix} 4 & 3 & 2 \\ 4 & \begin{bmatrix} sC_2(1+n) & -sC_2nm & -nSE_2n^2sC_2 \\ -sC_2(nm) & sC_2 & nSC_2 \\ -n^2nSC_2 & nsC_2 & n^2sC_2 \end{bmatrix} \\ 3 & \begin{bmatrix} 100s & 10s & -110s \\ 10s & s & -11s \\ -110s & -11s & 12s \end{bmatrix} \\ 2 & \begin{bmatrix} 100s & 10s & -110s \\ 10s & s & -11s \\ -110s & -11s & 12s \end{bmatrix} \end{bmatrix}$

① 端口压缩: 将多端网络的两个或更多端子连接在一起, 形成~个端子, 称为端口压缩 (约/列分别取和)

② 端口消除:

③ 端口接地: 直接删掉对应的行/列。

写不定导纳矩阵:

$Y_i(s) = \begin{bmatrix} 1 & 0 & 0 & -1 \\ 0 & 100s & -90s & -10s \\ -2 & -90s & 81s & 9s+2 \\ 1 & -10s & 19s & s-1 \end{bmatrix}$

(2) 写为定导纳矩阵 (以 3 为参考点)

$$Y_d(s) = \begin{bmatrix} 1 & 0 & -1 \\ 0 & 10s & -110s \\ -1 & -110s & 121s-2 \end{bmatrix}$$

消掉节点 4:

$$\begin{bmatrix} 1 + \frac{1}{121s-2} & -\frac{110s}{121s-2} \\ \frac{110s}{121s-2} & 110s - \frac{110s^2}{121s-2} \end{bmatrix}$$

整理得:

$$Y_{sc}(s) = \begin{bmatrix} \frac{121s-1}{121s-2} & -\frac{110s}{121s-2} \\ \frac{110s}{121s-2} & \frac{1210-220s}{121s-2} \end{bmatrix} \begin{bmatrix} \frac{1}{1+s-1} & -\frac{ns}{s-1} \\ \frac{ns}{s-1} & n^2s - \frac{n^2s}{s-1} \end{bmatrix}$$

解: (1) 列写 u_{c1} 所在基本割集的 KCL, i_{L2} 所在基本回路的 KVL.

$$-i_s + (-i_{L2}) + i_{R2} + i_{C2} + (-i_{C1}) = 0 \Rightarrow C_1 \frac{du_{C1}}{dt} = C_2 \frac{du_{C2}}{dt} - i_{L2} + i_{R2} - i_s$$

$$u_{L2} - u_{L1} - u_{C1} + u_s - R_1 i_{R1} = 0 \Rightarrow L_2 \frac{di_{L2}}{dt} = L_1 \frac{di_{L1}}{dt} + u_{C1} + R_1 i_{R1} - u_s$$

$$\dot{u}_{C2} = \dot{u}_s - \dot{u}_{C1} \quad \dot{i}_{L2} = -\dot{i}_s - \dot{i}_{L1}$$

$$\bar{i}_{R1} = \frac{u_s - u_{C1} - R_1 \dot{i}_{L2}}{R_1 + R_2}$$

$$\bar{i}_{R2} = \frac{u_s - u_{C1} + R_1 \dot{i}_{L2}}{R_1 + R_2} \quad \text{① 正负}$$

② 给出电源作用

③ 输出方程:

整理得:

$$\dot{u}_{C1} = -u_{C1} - \frac{1}{2} \dot{i}_{L2} + \frac{1}{2} \dot{u}_s + u_s - \dot{i}_s$$

$$\dot{i}_{L2} = \frac{1}{2} u_{C1} - \frac{1}{4} \dot{i}_{L2} - \frac{1}{2} \dot{i}_s - \frac{1}{2} u_s$$

写成矩阵形式:

$$\begin{bmatrix} \dot{u}_{C1} \\ \dot{i}_{L2} \end{bmatrix} = \begin{bmatrix} -1 & -\frac{1}{2} \\ \frac{1}{2} & -\frac{1}{4} \end{bmatrix} \begin{bmatrix} u_{C1} \\ \dot{i}_{L2} \end{bmatrix} + \begin{bmatrix} \frac{1}{2} & 0 \\ 0 & -\frac{1}{2} \end{bmatrix} \begin{bmatrix} \dot{u}_s \\ \dot{i}_s \end{bmatrix} + \begin{bmatrix} 1 & -1 \\ -\frac{1}{2} & 0 \end{bmatrix} \begin{bmatrix} u_s \\ \dot{i}_s \end{bmatrix}$$

(2)

$$\bar{i}_{R1} = \frac{1}{R_1 + R_2} u_s - \frac{1}{R_1 + R_2} u_{C1} - \frac{R_2}{R_1 + R_2} \dot{i}_{L2}$$

$$u_{C2} = -u_{C1} + u_s$$

$$\dot{i}_{L1} = -\dot{i}_{L2} - \dot{i}_s$$

$$\begin{bmatrix} \bar{i}_{R1} \\ \dot{i}_{L1} \\ u_{C2} \end{bmatrix} = \begin{bmatrix} -1 & -\frac{1}{2} \\ 0 & -1 \\ -1 & 0 \end{bmatrix} \begin{bmatrix} u_{C1} \\ \dot{i}_{L2} \end{bmatrix} + \begin{bmatrix} 1 & 0 \\ 0 & -1 \\ 1 & 0 \end{bmatrix} \begin{bmatrix} u_s \\ \dot{i}_s \end{bmatrix}$$

五解: (1) $C \frac{du_C}{dt} = \dot{i}_{R1} - \dot{i}_{L1}$

$L_1 \frac{di_{L1}}{dt} = -M \frac{di_{L2}}{dt} + u_C - R_2 \dot{i}_{L1} \Rightarrow$

$L_2 \frac{di_{L2}}{dt} = -M \frac{di_{L1}}{dt} + R_3 \dot{i}_{L2}$

$\dot{u}_C = -\dot{i}_{L1} + \dot{i}_{R1}$

$\dot{i}_{L1} = -\frac{1}{2} \dot{i}_{L2} + \frac{1}{2} u_C - \frac{1}{2} \dot{i}_{L1}$

$\dot{i}_{L2} = -\dot{i}_{L1} - \dot{i}_{L2}$

同时 $\dot{i}_{R1} = \frac{u_C - u_C}{R_1} \star$

整理得: $\dot{u}_C = -u_C - \dot{i}_{L1} + u_S$

$\dot{i}_{L1} = u_C - \dot{i}_{L1} + \dot{i}_{L2}$

$\dot{i}_{L2} = -u_C + \dot{i}_{L1} - 2\dot{i}_{L2}$

写成矩阵形式: $\begin{bmatrix} \dot{u}_C \\ \dot{i}_{L1} \\ \dot{i}_{L2} \end{bmatrix} = \begin{bmatrix} -1 & -1 & 0 \\ 1 & -1 & 1 \\ -1 & 1 & -2 \end{bmatrix} \begin{bmatrix} u_C \\ \dot{i}_{L1} \\ \dot{i}_{L2} \end{bmatrix} + \begin{bmatrix} 1 \\ 0 \\ 0 \end{bmatrix} u_S$


(2) 拉氏变换:

$sU_C(s) = -U_C(s) - I_{L1}(s) + U_S(s) + u_C(0_-)$

$sI_{L1}(s) = U_C(s) - I_{L1}(s) + I_{L2}(s) + i_{L1}(0_-)$

$sI_{L2}(s) = -U_C(s) + I_{L1}(s) - 2I_{L2}(s) + i_{L2}(0_-)$

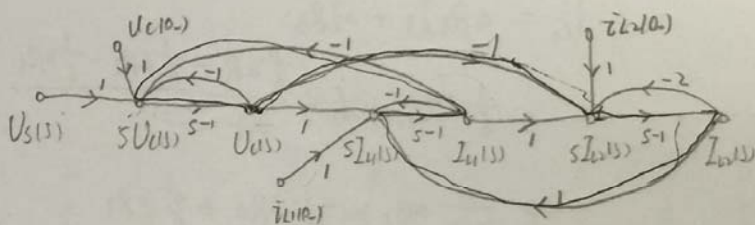$U_S(s) = \frac{3}{s} \quad (f(t) \text{ 的拉氏变换为 } \frac{1}{s}) \star$



(3) 图的行列式 $\Delta = 1 - [(-s^{-1}) + (-s^{-1}) + (-2s^{-1}) + (-s^{-2}) + s^{-2}] + (-s^{-1})(s^{-2}) + (-s^{-1})(-3s^{-1}) + (-s^{-1})(-2s^{-1})$

$(-s^{-2})(-2s^{-1}) - (-s^{-1})(-s^{-1})(-2s^{-1}) = 1 + 4s^{-1} + 3s^{-2} + 2s^{-2} + s^{-3} = 1 + 4s^{-1} + 5s^{-2} + 2s^{-3}$

$P_{m1} = s^{-2}$

$\Delta_{m1} = 1 + 2s^{-1}$

$T_1 = \frac{I_{L1}(s)}{U_S(s)}$

$= \frac{s^{-2} + 2s^{-3} - s^{-3}}{1 + 4s^{-1} + 5s^{-2} + 2s^{-3}} = \frac{s+1}{s^3 + 4s^2 + 5s + 2} \star$

$\Delta_{m2} = -s^{-3}$

$\Delta_{m2} = 1$

(4) 由 $u_C(0_-)$ 至 $u_C(s)$: $P_{1(1)} = s^{-1}$, $\Delta_{1(1)} = 1 - [(-s^{-1}) + (-2s^{-1})] - s^{-2} + (-s^{-1})(-2s^{-1}) = 1 + 3s^{-1} + s^{-2}$

由 $u_C(0_-)$ 至 $i_{L1}(s)$: $P_{1(2)} = s^{-2}$, $\Delta_{1(2)} = 1 + 2s^{-1}$

$P_{2(2)} = -s^{-3}$, $\Delta_{2(2)} = 1$

由 $u_C(0_-)$ 至 $i_{L2}(s)$: $P_{1(3)} = s^{-3}$, $\Delta_{1(3)} = 1$

$P_{2(3)} = -s^{-2}$

$\Delta_{2(3)} = 1 + s^{-1}$

$\dot{i}_{L1}(0_-) P_{1(2)} = \star$, $\Delta_{1(2)} = 1 + 2s^{-1}$

$P_{1(22)} = s^{-1}$, $\Delta_{1(22)} = 1 + 3s^{-1} + 2s^{-2}$

$P_{1(22)} = s^{-2}$, $\Delta_{1(22)} = 1 + s^{-1}$

$\dot{i}_{L2}(0_-) P_{1(3)} = -s^{-3}$, $\Delta_{1(3)} = 1$

$P_{1(23)} = s^{-2}$, $\Delta_{1(23)} = 1 + s^{-1}$

$P_{1(33)} = s^{-1}$, $\Delta_{1(33)} = 1 + 2s^{-1} + s^{-2}$

\star

$\Phi(s) = \begin{bmatrix} \frac{s^{-1} + 3s^{-2} + s^{-3}}{1 + 4s^{-1} + 5s^{-2} + s^{-3}} & \frac{-s^{-1}}{1 + 4s^{-1} + 5s^{-2} + s^{-3}} & \frac{-s^{-3}}{1 + 4s^{-1} + 5s^{-2} + s^{-3}} \\ \frac{s^{-2} + 2s^{-3}}{1 + 4s^{-1} + 5s^{-2} + s^{-3}} & \frac{s^{-1} + 3s^{-2}}{1 + 4s^{-1} + 5s^{-2} + s^{-3}} & \frac{s^{-2} + s^{-3}}{1 + 4s^{-1} + 5s^{-2} + s^{-3}} \\ \frac{s^{-3}}{1 + 4s^{-1} + 5s^{-2} + s^{-3}} & \frac{s^{-2} + s^{-3}}{1 + 4s^{-1} + 5s^{-2} + s^{-3}} & \frac{s^{-1} + 2s^{-2} + 2s^{-3}}{1 + 4s^{-1} + 5s^{-2} + s^{-3}} \end{bmatrix}$

$= \frac{1}{s^3 + 4s^2 + 5s + 2} \begin{bmatrix} u_C & \dot{i}_{L1} & \dot{i}_{L2} \\ 1 & s+1 & -1 \\ s+1 & s^2+3s+2 & s+1 \\ s & s+2 & s^2+3s+2 \end{bmatrix}$

(5) $U_C(s) = \Phi_{11}(s) u_C(0_-) + \Phi_{12}(s) \dot{i}_{L1}(0_-) + \Phi_{13}(s) \dot{i}_{L2}(0_-) = \frac{2s^2 + 6s + 2}{s^3 + 4s^2 + 5s + 1} (s+1)^2 (s+2) + T_S U_S(s)$

$s(s+2)^2 + (s+1)$


六、解：(1) 列写节点方程：

$$(G_1 + G_2) U_{n1} - G_2 U_{n2} = I_s$$

$$-G_2 U_{n1} + (G_2 + G_3) U_{n2} = 0$$

解： $U_{n1} = \frac{11}{3}$ $U_{n2} = 1$ $I_1 = \frac{U_{n1}}{R_1} = \frac{\frac{11}{3}}{2} = \frac{11}{6}$ $I_2 = \frac{U_{n1} - U_{n2}}{R_2} = \frac{\frac{11}{3} - 1}{16} = \frac{1}{6}$

增量网络：

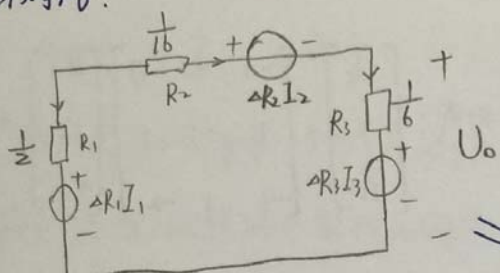

★ U_o 应包含新增电压源！

$$I_3 = \frac{U_{n2}}{R_3} = \frac{1}{6}$$

$$\Rightarrow \Delta I(R_1 + R_2 + R_3) = \Delta R_1 I_1 - \Delta R_2 I_2 - \Delta R_3 I_3$$

★ 新网络 } 节点电压
导 (易于求解即可)

$$\begin{aligned} U_o &= \Delta R_3 I_3 + \Delta I R_3 \\ &= \frac{1}{6} \Delta R_3 + 6 \times \frac{\frac{11}{6} \Delta R_1 - \frac{1}{6} \Delta R_2 - \frac{1}{6} \Delta R_3}{24} = \frac{1}{6} \Delta R_3 + \frac{11}{24} \Delta R_1 - \frac{1}{24} \Delta R_2 - \frac{1}{24} \Delta R_3 \\ &= \frac{11}{24} \Delta R_1 - \frac{1}{24} \Delta R_2 + \frac{1}{8} \Delta R_3 \end{aligned}$$

$$\therefore \hat{S}_{R_1}^{U_o} = \frac{11}{24} = 0.4583$$

$$\hat{S}_{R_2}^{U_o} = -\frac{1}{24} = -0.04167$$

$$\hat{S}_{R_3}^{U_o} = \frac{1}{8} = 0.125$$

$$\hat{S}_R^T = \frac{\partial T}{\partial R_1} = \frac{\partial}{\partial R_1} \left(\frac{U_o}{I_s} \right) = \frac{1}{I_s} \hat{S}_{R_1}^{U_o} = 0.2292$$

$$\Delta I(R_1 R_2)$$