

2013.

一. 解: 端口电流电压关系:

$$u(t) = \frac{1}{C} \int_{t_0}^t i(t) dt + \frac{z}{C}(t-t_0)$$

设输入为  $v(t) = u(t)$ , 输出  $y(t) = i(t)$ .

$$\text{则端口输入-输出算子: } P(v, y) = v - \frac{1}{C} \int_{t_0}^t y dt + \frac{z}{C}(t-t_0) = 0$$

$$\text{则对于 } \hat{v}, \hat{y}: P(\hat{v}, \hat{y}) = \hat{v} - \frac{1}{C} \int_{t_0}^t \hat{y} dt + \frac{z}{C}(t-t_0) = 0$$

$$\text{而对于 } v+\hat{v}, y+\hat{y}: P(v+\hat{v}, y+\hat{y}) = v+\hat{v} - \frac{1}{C} \int_{t_0}^t (y+\hat{y}) dt + \frac{z}{C}(t-t_0) \neq 0$$

不满足可加性, 故非端口型线性网络.

二. 解: ① VCCS 对原始不定导纳矩阵贡献为:

$$\begin{matrix} & 5 & 3 & & \\ 4 & \begin{bmatrix} g_m & -g_m \end{bmatrix} & & & \\ & & & 3 & 5 \\ 3 & \begin{bmatrix} -g_m & g_m \end{bmatrix} & & & \\ & & & 4 & \begin{bmatrix} -g_m & g_m \end{bmatrix} \end{matrix}$$

② 回转器对二端导纳矩阵的贡献:

$$\begin{matrix} & 5 & 3 & 2 & 3' \\ 5 & \begin{bmatrix} 0 & 0 & g & -g \end{bmatrix} & & & \\ 3 & \begin{bmatrix} 0 & 0 & -g & g \end{bmatrix} & & & \\ 2 & \begin{bmatrix} -g & g & 0 & 0 \end{bmatrix} & & & \\ 3' & \begin{bmatrix} g & -g & 0 & 0 \end{bmatrix} & & & \end{matrix} \Rightarrow \begin{matrix} & 5 & 3 & 2 \\ 5 & \begin{bmatrix} 0 & -g & g \end{bmatrix} & & \\ 3 & \begin{bmatrix} g & 0 & -g \end{bmatrix} & & \\ 2 & \begin{bmatrix} -g & g & 0 \end{bmatrix} & & \end{matrix} = \begin{matrix} & 2 & 3 & 5 \\ 2 & \begin{bmatrix} 0 & g & -g \end{bmatrix} & & \\ 3 & \begin{bmatrix} -g & 0 & g \end{bmatrix} & & \\ 5 & \begin{bmatrix} g & -g & 0 \end{bmatrix} & & \end{matrix}$$

原始不定导纳矩阵:

$$Y_{(11)} = \begin{bmatrix} \frac{1}{R_1} & 0 & 0 & -\frac{1}{R_1} & 0 \\ 0 & 0 & g & 0 & -g \\ 0 & -g & g_m & 0 & g-g_m \\ -\frac{1}{R_1} & 0 & -g_m & \frac{1}{R_1}+sC_2 & g_m-sC_2 \\ 0 & g & -g & -sC_2 & sC_2 \end{bmatrix}$$

以节点3为参考节点, 得定导纳矩阵:

$$Y_{d(11)} = \begin{bmatrix} \frac{1}{R_1} & 0 & -\frac{1}{R_1} & 0 \\ 0 & 0 & 0 & -g \\ -\frac{1}{R_1} & 0 & \frac{1}{R_1}+sC_2 & g_m-sC_2 \\ 0 & g & -sC_2 & sC_2 \end{bmatrix}$$

消节点⑤:  $\begin{bmatrix} \frac{1}{R_1} & 0 & -\frac{1}{R_1} \\ 0 & \frac{g^2}{sC_2} & -g \\ -\frac{1}{R_1} & \frac{g(sC_2-g_m)}{sC_2} & \frac{1}{R_1}+g_m \end{bmatrix}$



消节点④:  $Y_{sc(111)} = \frac{1}{R_1} - \frac{1}{R_1^2} \times \frac{R_1}{1+R_1g_m} = \frac{g_m}{1+R_1g_m}$   
 $Y_{sc(21)} = -\frac{g}{R_1} \times \frac{R_1}{1+R_1g_m} = -\frac{g}{1+R_1g_m}$

$$Y_{sc(12)} = \frac{1}{R_1} \times \frac{g(sC_2 - g_m)}{sC_2} \times \frac{R_1}{1 + R_1 g_m} = \frac{g(sC_2 - g_m)}{sC_2(1 + R_1 g_m)}$$


$$Y_{sc(22)} = \frac{g^2}{sC_2} + \frac{g^2(sC_2 - g_m)}{sC_2} \times \frac{R_1}{1 + R_1 g_m} = \frac{g^2(1 + R_1 sC_2)}{sC_2(1 + R_1 g_m)}$$

短路导纳矩阵:  $Y_{sc}(s) = \begin{bmatrix} \frac{g_m}{1 + R_1 g_m} & \frac{g(sC_2 - g_m)}{sC_2(1 + R_1 g_m)} \\ \frac{-g}{1 + R_1 g_m} & \frac{g^2(1 + R_1 sC_2)}{sC_2(1 + R_1 g_m)} \end{bmatrix}$




四、解: (1) 短路导纳矩阵:

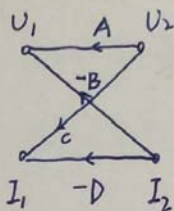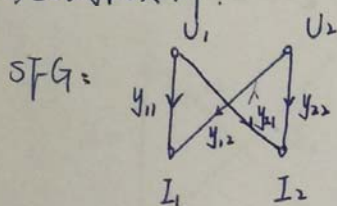

将  $U_1, I_2$  倒向:

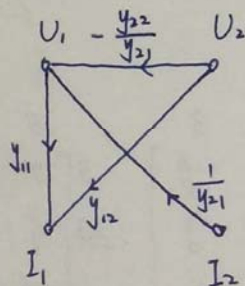

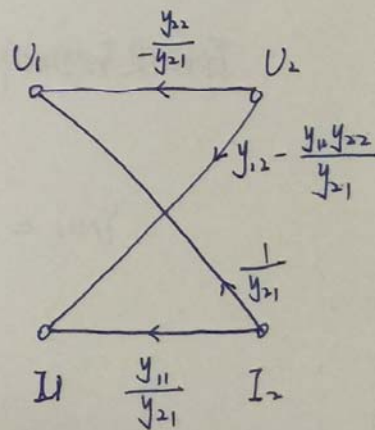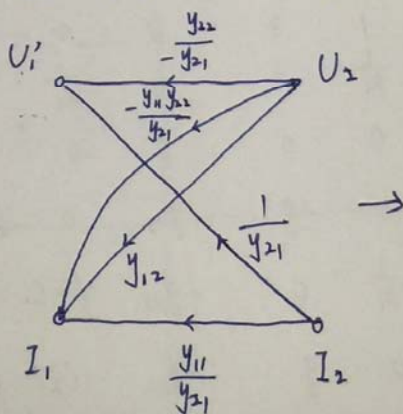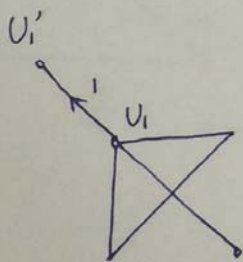$I_1$  与  $I_2$  缺少支路、 $U_1, I_2$  多一条支路。建 newNode  $U_1'$ , 消去  $U_1$ .



$$A = -\frac{y_{22}}{y_{21}}$$

$$B = \frac{-1}{y_{21}}$$



$$C = y_{12} - \frac{y_{11}y_{22}}{y_{21}}$$

$$D = -\frac{y_{11}}{y_{21}}$$




(2) 开路阻抗矩阵:

SFG:

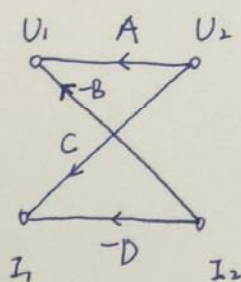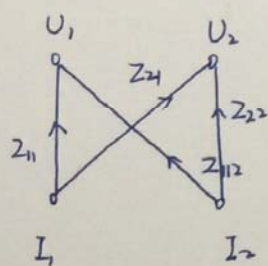


U-I 流向:

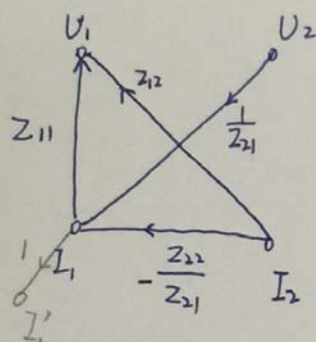

$U_1, U_2$  少一条

$U_1, I_1$  多一条

新建  $I_1'$ , 消掉  $I_1$  节点:

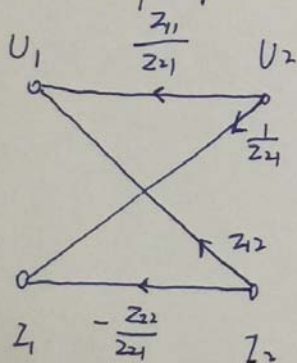

$$A = \frac{Z_{11}}{Z_{21}}$$

$$B = -Z_{12}$$

$$C = \frac{1}{Z_{21}}$$

$$D = \frac{Z_{22}}{Z_{21}}$$